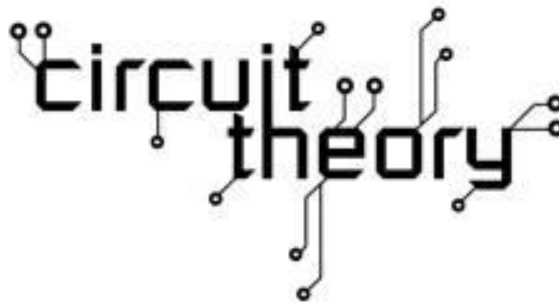




**University of Western Attica  
Faculty of Engineering  
Department of Informatics and Computer Engineering**

**Circuit Theory Lab Exercises**

**1st EXERCISE**



**Notes 2020, Voutsinas Stylianos  
Material revision, Editor 2021, Christos Kampouris**

**ATHENS  
2021**

## **1.1 Laboratory part**

### **1.2 Circuits - theorems - basic laws**

- As a circuit, the set of electrical sources and passive or active elements, which are connected to each other, is characterized.
- A branch is any part of the circuit that has its elements connected in series.
- A loop is any closed path of a circuit, designed so that the path does not pass through the same point twice.
- A node is the point where two or more branches join.

#### ***Kirchhoff's first law***

The algebraic sum of all the intensities of the currents flowing into and out of the node is zero

#### ***Kirchhoff's second law***


The sum of all potential differences across the individual branches of a loop is zero

#### ***Ohm's Law***

The intensity of the current  $I$  is proportional to the potential difference with a ratio factor of  $1/R$

<b>1. 3.1 : Kirchoff 's 1st law .</b>
---------------------------------------


You experimentally verified through Figure 1 Kirchhoff's 1st law (the algebraic sum of all intensities of the currents flowing into and out of the node equals zero). Record your measurements and reasoning.

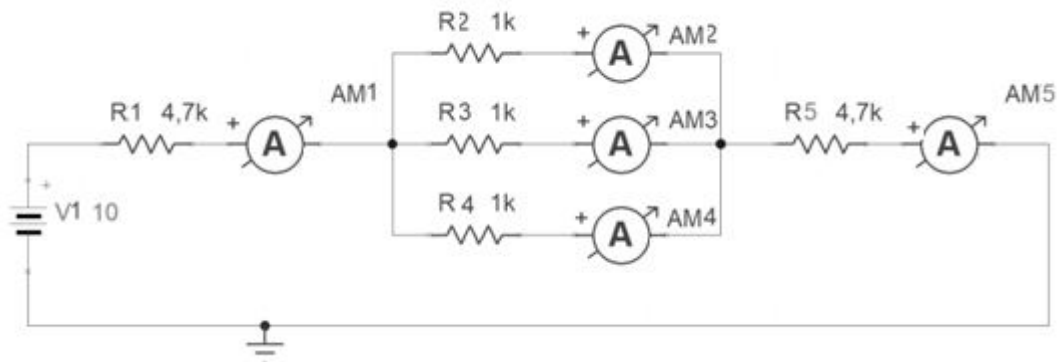

**Figure 1**

### 1.3.2 : Kirchhoff's 2nd law .

You experimentally verified through figure 2 Kirchhoff's 2nd law (the sum of all potential differences in the individual branches of a loop is equal to zero). Record your measurements and reasoning. Prove the simulation part based on the trend calculation formulas.

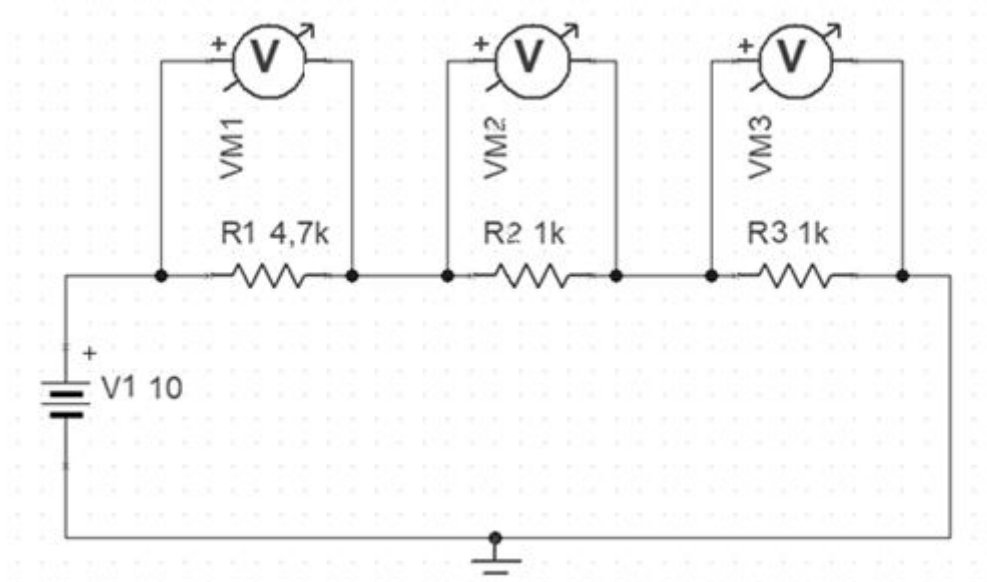

**Figure 2**

### 1. 3.3 : Ohm's law .


K, change

[illegible][illegible][illegible]

### 1. 3.4 : Connecting a resistor as a potentiometer.

Implement the circuit of Figure 4. Change the value of the variable resistor and complete the table below. Comment.

Helpful Note: The circuit below uses voltage divider circuitry.

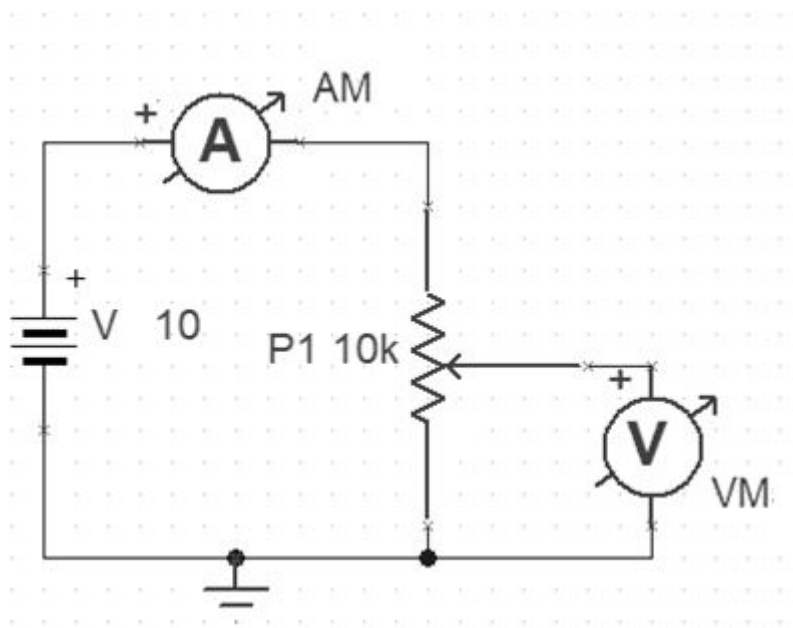


*Figure 4*

Resistance (R) %	10	20	30	40	50	60	70	80	90	100
Voltage ( V )										

### 1.5. 5 : Connecting a resistor as a dimmer.

Implement the circuit of Figure 5. Change the value of the variable resistor and complete the table below.

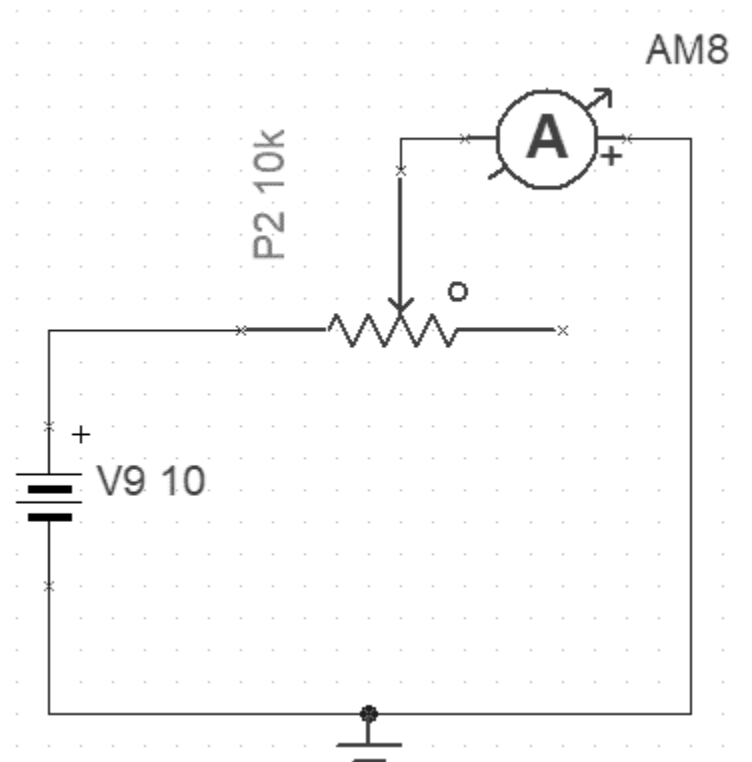

*Figure 5*

Resistance (R) %	10	20	30	40	50	60	70	80	90	100
Intensity (I)										

## 1.6 Questions

- What will happen in Figure 5 if the variable resistor goes to 0%? You calculated the current that will flow through the resistor. Is there a way to fix this particular problem?

- The voltage measurement in figure 3, would it be better to include the voltage drop across the resistor  $R_4$  and the ammeter? Justify.
- Consider a voltage divider with  $R_1 = R_2 = 1\text{ K}\Omega$ . We connect a load  $R_L = 10\Omega$ . What will happen? Suggest a way to solve it.